

**2022**

**COMPUTER SCIENCE — GENERAL**

**Paper : GE/CC-1**

**(Computer Fundamentals and Digital Logic Design)**

**Full Marks : 50**

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

Answer **question no. 1** and **any four** questions from the rest.

1. Answer **any five** questions from the following : 2×5
- (a) Define BIOS.
  - (b) Perform the following conversions :
    - (i)  $(10011011)_2 = (?)_{16}$
    - (ii)  $(236)_8 = (?)_2$
  - (c) What is the advantage of using cache memory?
  - (d) Draw the truth table of a half-adder and draw its logic diagram.
  - (e) Write any two advantages of high level language.
  - (f) Find the 2's complement of the number  $(101101)_2$ .
  - (g) State any two characteristics of a multimedia software.
  - (h) Draw a right shift register with a suitable illustration.
2. Simplify the following functions using Karnaugh map method and implement the resultant simplified function using basic gates only.
- (a)  $F(A, B, C, D) = \sum(0, 2, 3, 4, 8, 12, 15)$
  - (b)  $F(A, B, C, D) = \prod(1, 3, 4, 5, 7, 11, 12, 15)$  (3+2)+(3+2)
3. (a) Design a 3-to-8 decoder circuit.
- (i) Draw the truth table.
  - (ii) Draw the logic diagram.
- (b) Design a 3 bit binary subtractor circuit (Draw only the truth table and logic diagram). (3+3)+4

**Please Turn Over**

4. (a) Design an even parity generator (Draw the truth table and logic diagram).  
(b) Draw the logic diagram of a T flip-flop, and write its characteristic table. (2+2)+(3+3)
5. (a) State the two variable De Morgan's Laws. Prove these using truth tables.  
(b) What is a universal gate? Prove that NAND is a universal gate. (2+4)+(1+3)
6. (a) Draw the logic diagram of an edge triggered RS flip-flop and draw its excitation table.  
(b) Draw the logic diagram of a 4 bit ring counter. (4+2)+4
7. Design a 4 bit asynchronous up-counter.  
(a) Draw the logic diagram.  
(b) Draw the truth table.  
(c) Draw the timing diagram. 3+3+4
8. Write short notes on **any two** of the following : 5×2  
(a) System software  
(b) Computer virus  
(c) Compilers and Interpreters  
(d) Seven Segment Display.
-